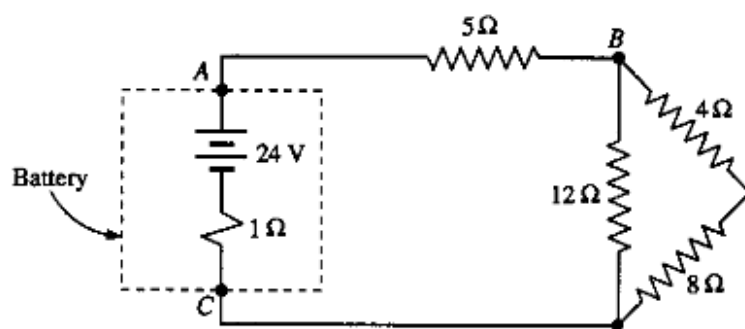



AP Physics 2 – Chapter 18 Circuit Homework



A battery with an emf of 24 volts and an internal resistance of 1 ohm is connected to an external circuit as shown above.


Determine each of the following:

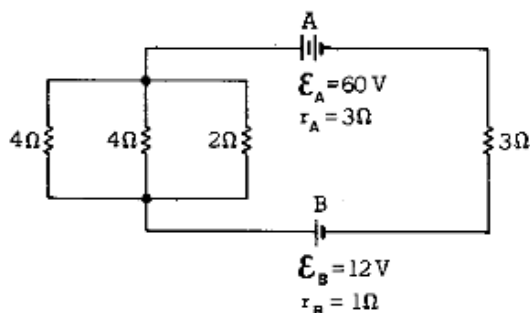- the equivalent resistance of the combination of the 4-ohm, 8-ohm, and 12-ohm resistors
- the current in the 5-ohm resistor
- the terminal voltage, V_{AC} , of the battery
- the rate at which energy is dissipated in the 12-ohm resistor
- the magnitude of the potential difference V_{BC}
- the power delivered by the battery to the external circuit




A circuit consists of battery A of emf $\mathcal{E}_A = 60$ volts and internal resistance $r_A = 3$ ohms; battery B of emf $\mathcal{E}_B = 12$ volts and internal resistance $r_B = 1$ ohm; and four resistors connected as shown in the diagram above.

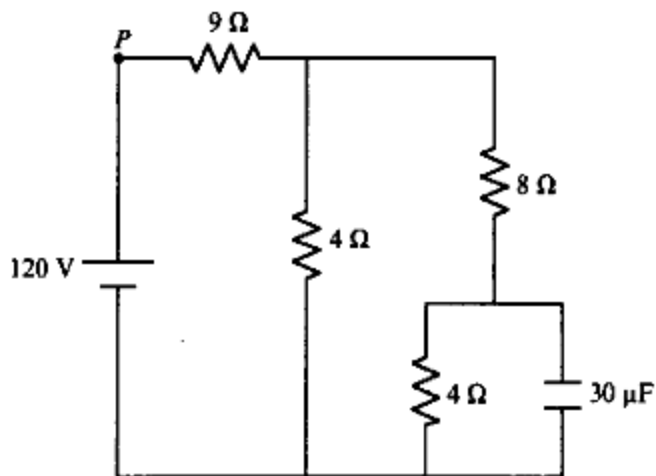- Calculate the current in the 2-ohm resistor.
- Calculate the power dissipated in the 3-ohm resistor.
- Calculate the terminal voltage of battery B.



In the circuit shown above, the battery has been connected for a long time so that the currents have steady values. Given these conditions, calculate each of the following.

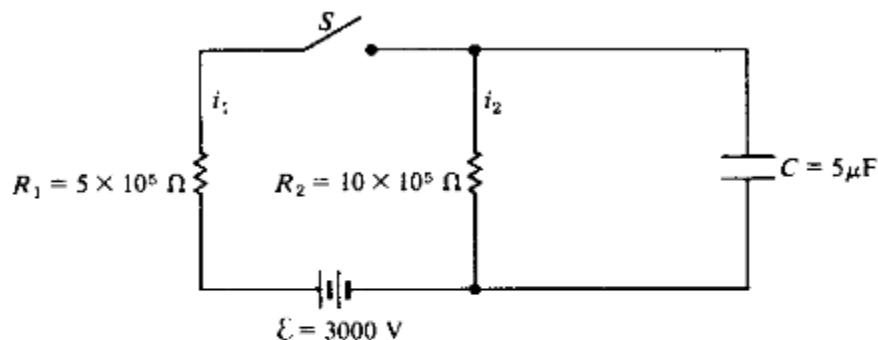- The current in the 9-ohm resistor
- The current in the 8-ohm resistor
- The potential difference across the 30-microfarad capacitor
- The energy stored in the 30-microfarad capacitor



In the circuit shown above, i_1 and i_2 are the currents through resistors R_1 and R_2 , respectively. V_1 , V_2 , and V_C are the potential differences across resistor R_1 , resistor R_2 , and capacitor C , respectively. Initially the capacitor is uncharged.

- Calculate the current i_1 immediately after switch S is closed.

Assume switch S has been closed for a long time.

- Calculate the current i_2 .
- Calculate the charge Q on the capacitor.
- Calculate the energy U stored in the capacitor.