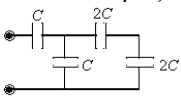


## AP Physics C: Unit II/III Practice

## Multiple Choice

Identify the choice that best completes the statement or answers the question.

- \_\_\_\_\_ 1. A  $0.25\text{-}\mu\text{F}$  capacitor is connected to a  $400\text{-V}$  battery. Find the charge on the capacitor.  
 a.  $1.2 \times 10^{-12}\text{ C}$     b.  $1.0 \times 10^{-4}\text{ C}$     c.  $0.040\text{ C}$     d.  $0.020\text{ C}$
- \_\_\_\_\_ 2. A parallel-plate capacitor has a capacitance of  $20\ \mu\text{F}$ . What potential difference across the plates is required to store  $7.2 \times 10^{-4}\text{ C}$  on this capacitor?  
 a.  $36\text{ V}$     b.  $2.2 \times 10^{-2}\text{ V}$     c.  $1.4 \times 10^{-8}\text{ V}$     d.  $18\text{ V}$
- \_\_\_\_\_ 3. A  $20\text{-}\mu\text{F}$  capacitor has a  $1000\text{-V}$  power supply. What is the charge on the capacitor?  
 a.  $10\text{ mC}$     b.  $20\text{ mC}$     c.  $40\text{ mC}$     d.  $80\text{ mC}$
- \_\_\_\_\_ 4. Two capacitors with capacitances of  $1.5$  and  $0.25\ \mu\text{F}$ , respectively, are connected in parallel. The system is connected to a  $50\text{-V}$  battery. What charge accumulates on the  $1.5\text{-}\mu\text{F}$  capacitor?  
 a.  $100\ \mu\text{C}$     b.  $75\ \mu\text{C}$     c.  $50\ \mu\text{C}$     d.  $33\ \mu\text{C}$     e.  $25\ \mu\text{C}$
- \_\_\_\_\_ 5. Two capacitors with capacitances of  $1.0$  and  $0.50\ \mu\text{F}$ , respectively, are connected in series. The system is connected to a  $100\text{-V}$  battery. What charge accumulates on the  $1.0\text{-}\mu\text{F}$  capacitor?  
 a.  $150\ \mu\text{C}$     b.  $100\ \mu\text{C}$     c.  $50\ \mu\text{C}$     d.  $33\ \mu\text{C}$     e.  $25\ \mu\text{C}$
- \_\_\_\_\_ 6. If  $C = 36\ \mu\text{F}$ , determine the equivalent capacitance for the combination shown.  
  
 a.  $36\ \mu\text{F}$     b.  $32\ \mu\text{F}$     c.  $28\ \mu\text{F}$     d.  $24\ \mu\text{F}$     e.  $20\ \mu\text{F}$
- \_\_\_\_\_ 7. Two capacitors,  $1.5\ \mu\text{F}$  and  $0.25\ \mu\text{F}$ , respectively, are connected in parallel. The system is connected to a  $50\text{-V}$  battery. What electrical potential energy is stored in the  $1.5\text{-}\mu\text{F}$  capacitor?  
 a.  $0.5 \times 10^{-3}\text{ J}$     b.  $1.2 \times 10^{-3}\text{ J}$     c.  $1.9 \times 10^{-3}\text{ J}$     d.  $10 \times 10^{-3}\text{ J}$     e.  $19 \times 10^{-3}\text{ J}$
- \_\_\_\_\_ 8. Two capacitors,  $1.0\ \mu\text{F}$  and  $0.50\ \mu\text{F}$ , are connected in series. The system is connected to a  $100\text{-V}$  battery. What electrical potential energy is stored in the  $1.0\text{-}\mu\text{F}$  capacitor?  
 a.  $0.065 \times 10^{-3}\text{ J}$     b.  $4.3 \times 10^{-3}\text{ J}$     c.  $0.80 \times 10^{-3}\text{ J}$     d.  $5.6 \times 10^{-4}\text{ J}$
- \_\_\_\_\_ 9. A "sandwich" is constructed of two flat pieces of metal ( $2.00\text{ cm}$  on a side) with a  $2.00\text{-mm}$ -thick piece of a dielectric called Rutile ( $\kappa = 100$ ) in between them. What is the capacitance?  
 a.  $177\text{ pF}$     b.  $885\text{ nF}$     c.  $8.85\ \mu\text{F}$     d.  $100\ \mu\text{F}$     e.  $177\ \mu\text{F}$

\_\_\_\_\_ 10. Two cylindrical resistors are made of the same material and have the same resistance. The resistors,  $R_1$  and  $R_2$ , have different radii,  $r_1$  and  $r_2$ , and different lengths,  $L_1$  and  $L_2$ . Which of the following relative values for radii and lengths would result in equal resistances?

- a.  $r_1 = r_2$  and  $L_1 = 2L_2$                       c.  $r_1 = r_2$  and  $4L_1 = L_2$   
 b.  $2r_1 = r_2$  and  $L_1 = 2L_2$                       d.  $2r_1 = r_2$  and  $4L_1 = L_2$


\_\_\_\_\_ 11. A 500-W heater carries a current of 4.0 A. How much does it cost to operate the heater for 30 min if electrical energy costs 6.0 cents per kWh?

- a. 1.5 cents      b. 9.0 cents      c. 18 cents      d. 36 cents      e. 95 cents

\_\_\_\_\_ 12. When a 24.0- $\Omega$  resistor is connected across a 12.0-V battery, a current of 482 mA flows. What is the power output delivered by the emf of the battery?

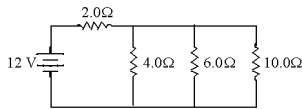- a. 0.21 W      b. 5.57 W      c. 5.78 W      d. 6.00 W      e. 7.19 W

\_\_\_\_\_ 13. Three resistors connected in parallel have values of 4, 6 and 10  $\Omega$ , respectively. If this combination is connected in series with a 12V battery and a 2  $\Omega$  resistor, what is the current in the 10  $\Omega$  resistor?



- a. 0.59 A      b. 1.0 A      c. 11 A      d. 16 A      e. 23 A


\_\_\_\_\_ 14. Two resistors of values 6.0 and 12.0  $\Omega$  are connected in parallel. This combination in turn is hooked in series with a 2.0- $\Omega$  resistor and a 24-V battery. What is the current in the 2- $\Omega$  resistor?

- a. 2.0 A      b. 4.0 A      c. 6.0 A      d. 12 A      e. 20 A

\_\_\_\_\_ 15. Two resistors of values 6.0 and 12.0  $\Omega$  are connected in parallel. This combination in turn is hooked in series with a 4.0- $\Omega$  resistor and a 24-V battery. What is the current in the 6- $\Omega$  resistor?

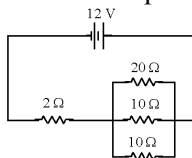
- a. 2.0 A      b. 3.0 A      c. 6.0 A      d. 12 A      e. 21 A

\_\_\_\_\_ 16. How much power is being dissipated by one of the 10- $\Omega$  resistors?



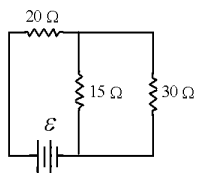
- a. 24 W      b. 9.6 W      c. 16 W      d. 6.4 W      e. 8.2 W

\_\_\_\_\_ 17. If  $\epsilon = 9.0$  V, what is the current in the 15- $\Omega$  resistor?



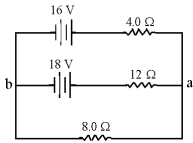
- a. 0.20 A      b. 0.30 A      c. 0.10 A      d. 0.26 A      e. 0.15 A

\_\_\_\_\_ 18. What is the current through the 8- $\Omega$  resistor?



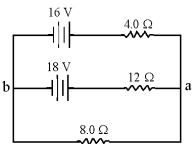
- a. 1.0 A      b. 0.50 A      c. 1.5 A      d. 2.0 A      e. 2.5 A

\_\_\_\_\_ 19. What is the potential difference between points a and b?



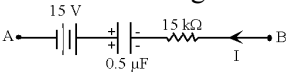
- a. 6 V      b. 8 V      c. 12 V      d. 24 V      e. 27 V

\_\_\_\_\_ 20. In the circuit segment shown if  $I = 7 \text{ mA}$  and  $Q = 50 \mu\text{C}$ , what is the potential difference,  $V_A - V_B$ ?



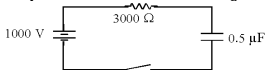- a. -40 V      b. +40 V      c. +20 V      d. -20 V      e. -15 V

\_\_\_\_\_ 21. A 1000 V battery, a 3000  $\Omega$  resistor and a 0.5  $\mu\text{F}$  capacitor are connected in series with a switch. The capacitor is initially uncharged. What is the value of the current the moment after the switch is closed?



- a. 0.39 A      b. 0.33 A      c. 0.84 A      d. 2 000 A      e. 1.0 A

\_\_\_\_\_ 22. A series  $RC$  circuit is made from a battery, a switch, a resistor, and a 3  $\mu\text{F}$  capacitor, and has a time constant of 9 ms. If a 6  $\mu\text{F}$  is added in series to the 3  $\mu\text{F}$  capacitor, what is the time constant?

- a. 4.0 ms      b. 6.0 ms      c. 10 ms      d. 16 ms

**AP Physics C: Unit II/III Practice  
Answer Section**

**MULTIPLE CHOICE**

1. B
2. A
3. B
4. B
5. D
6. D
7. C
8. D
9. A
10. D
11. A
12. C
13. A
14. B
15. A
16. D
17. A
18. C
19. C
20. D
21. B
22. B