

Chapter 26 - Problem Day

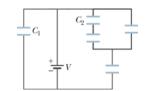
12. In the figure, the battery has a potential difference of V = 10.0 V and the five capacitors each have a capacitance of 10.0 μ F. What is the charge on (a) capacitor 1 and (b) capacitor 2?



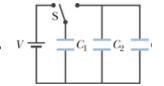
20. In the figure, V = 10 V, $C_1 = 10$ μ F, and $C_2 = C_3 = 20$ μ F. Switch S is first thrown to the left side until capacitor 1 reaches equilibrium. Then the switch is thrown to the right. When equilibrium is again reached, how much charge is on capacitor 1?



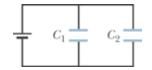
21. In the figure, two parallel-plate capacitors (with air between the plates) are connected to a battery. Capacitor 1 has a plate area of 1.5 cm² and an electric field of magnitude 2000 V/m. Capacitor 2 has a plate area of 0.70 cm² and an electric field of magnitude 1500 V/m. What is the total charge on the two capacitors?



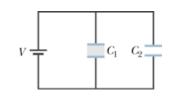- 30. A parallel-plate air-filled capacitor having area 40 cm² and plate spacing 1.0 mm is charged to a potential difference of 600 V. Find (a) the capacitance, (b) the magnitude of the charge on each plate, (c) the stored energy, and (d) the electric field between the plates.
- 35. The parallel plates of a capacitor, with a plate area of 8.5 cm² and an air-filled separation of 3 mm, are charged by a 6 V battery. They are then disconnected from the battery and pulled apart (without discharge) to a separation of 8 mm. Find (a) the potential difference between the plates, (b) the initial stored energy, (c) the final stored energy, and (d) the work required to separate the plates.
- 42. An air-filled parallel-plate capacitor has a capacitance of 1.3 pF. The separation of the plates is doubled, and wax is inserted between. The new capacitance is 2.6 pF. Find the dielectric constant of the wax.
- 44. In the figure, how much charge is stored on the parallel-plate capacitors by the 12.0 V battery? One is filled with air, and the other is filled with a dielectric for which $\kappa = 3.00$; both capacitors have a plate area of 5.00×10^{-3} m² and a plate separation of 2.00 mm.



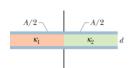48. The figure shows a parallel-plate capacitor with a plate area A = 5.56 cm² and separation d = 5.56 mm. The left half of the gap is filled with material of dielectric constant $\kappa_1 = 7$; the right half is filled with material of dielectric constant $\kappa_2 = 12$. What is the capacitance?



Chapter 26 Answers

- 12a) 100 μC
- 12b) 20 μC
- 20) 20 μC
- 21) 3.6 pC
- 30a) 35 pF
- 30b) 21 nC
- 30c) 6.3 μJ
- 30d) $6.00 \times 10^5 \text{ V/m}$
- 35a) 16 V
- 35b) 4.51×10⁻¹¹ J
- 35c) $1.20 \times 10^{-10} \text{ J}$
- 35d) $7.52 \times 10^{-11} \text{ J}$
- 42) 4
- 44) 1.06 × 10⁻⁹ C
- 48) $8.41 \times 10^{-12} \text{ F}$