

Chapter 26 Homework Problems

3. (a) When a battery is connected to the plates of a $3.00\text{-}\mu\text{F}$ capacitor, it stores a charge of $27.0\ \mu\text{C}$. What is the voltage of the battery? (b) If the same capacitor is connected to another battery and $36.0\ \mu\text{C}$ of charge is stored on the capacitor, what is the voltage of the battery?

5. **M** A 50.0-m length of coaxial cable has an inner conductor that has a diameter of $2.58\ \text{mm}$ and carries a charge of $8.10\ \mu\text{C}$. The surrounding conductor has an inner diameter of $7.27\ \text{mm}$ and a charge of $-8.10\ \mu\text{C}$. Assume the region between the conductors is air. (a) What is the capacitance of this cable? (b) What is the potential difference between the two conductors?

7. When a potential difference of $150\ \text{V}$ is applied to the plates of a parallel-plate capacitor, the plates carry a surface charge density of $30.0\ \text{nC}/\text{cm}^2$. What is the spacing between the plates?

12. **S Review.** A small object of mass m carries a charge q and is suspended by a thread between the vertical plates of a parallel-plate capacitor. The plate separation is d . If the thread makes an angle θ with the vertical, what is the potential difference between the plates?

13. Two capacitors, $C_1 = 5.00\ \mu\text{F}$ and $C_2 = 12.0\ \mu\text{F}$, are connected in parallel, and the resulting combination is connected to a 9.00-V battery. Find (a) the equivalent capacitance of the combination, (b) the potential difference across each capacitor, and (c) the charge stored on each capacitor.

14. **What If?** The two capacitors of Problem 13 ($C_1 = 5.00\ \mu\text{F}$ and $C_2 = 12.0\ \mu\text{F}$) are now connected in series and to a 9.00-V battery. Find (a) the equivalent capacitance of the combination, (b) the potential difference across each capacitor, and (c) the charge on each capacitor.

18. Find (a) the equivalent capacitance of the capacitors in Figure P26.18, (b) the charge on each capacitor, and (c) the potential difference across each capacitor.

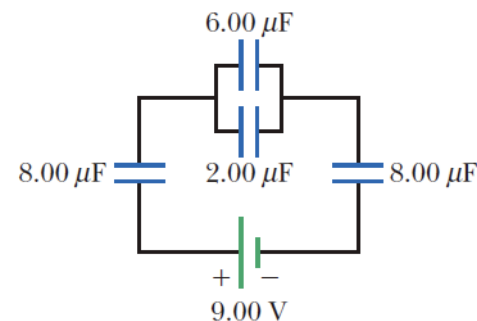


Figure P26.23

24. **M** Consider the circuit shown in Figure P26.24, where $C_1 = 6.00\ \mu\text{F}$, $C_2 = 3.00\ \mu\text{F}$, and $\Delta V = 20.0\ \text{V}$. Capacitor C_1 is first charged by closing switch S_1 . Switch S_1 is then opened, and the charged capacitor is connected to the uncharged capacitor by closing S_2 . Calculate (a) the initial charge acquired by C_1 and (b) the final charge on each capacitor.


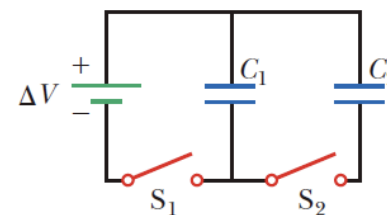


Figure P26.24

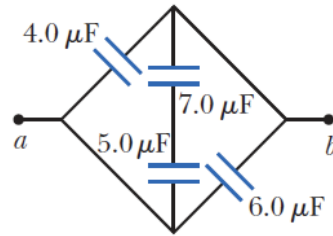29. Find the equivalent capacitance between points a and b in the combination of capacitors shown in Figure P26.29.



31. A 12.0-V battery is connected to a capacitor, resulting in $54.0 \mu\text{C}$ of charge stored on the capacitor. How much energy is stored in the capacitor?

39. **Review.** The circuit in Figure P26.39 consists of two identical, parallel metal plates connected to identical metal springs, a switch, and a 100-V battery. With the switch open, the plates are uncharged, are separated by a distance $d = 8.00 \text{ mm}$, and have a capacitance $C = 2.00 \mu\text{F}$. When the switch is closed, the distance between the plates decreases by a factor of 0.500. (a) How much charge collects on each plate? (b) What is the spring constant for each spring?


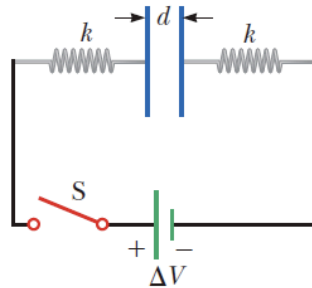


Figure P26.39

45. Determine (a) the capacitance and (b) the maximum potential difference that can be applied to a Teflon-filled parallel-plate capacitor having a plate area of 1.75 cm^2 and a plate separation of 0.0400 mm .

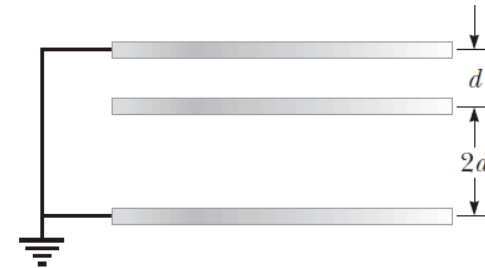56. **S** Two large, parallel metal plates, each of area A , are oriented horizontally and separated by a distance $3d$. A grounded conducting wire joins them, and initially each plate carries no charge. Now a third identical plate carrying charge Q is inserted between the two plates, parallel to them and located a distance d from the upper plate as shown in Figure P26.56. (a) What induced charge appears on each of the two original plates? (b) What potential difference appears between the middle plate and each of the other plates?



59. **M** A parallel-plate capacitor is constructed using a dielectric material whose dielectric constant is 3.00 and whose dielectric strength is $2.00 \times 10^8 \text{ V/m}$. The desired capacitance is $0.250 \mu\text{F}$, and the capacitor must withstand a maximum potential difference of 4.00 kV. Find the minimum area of the capacitor plates.
65. A capacitor of unknown capacitance has been charged to a potential difference of 100 V and then disconnected from the battery. When the charged capacitor is then connected in parallel to an uncharged $10.0\text{-}\mu\text{F}$ capacitor, the potential difference across the combination is 30.0 V. Calculate the unknown capacitance.